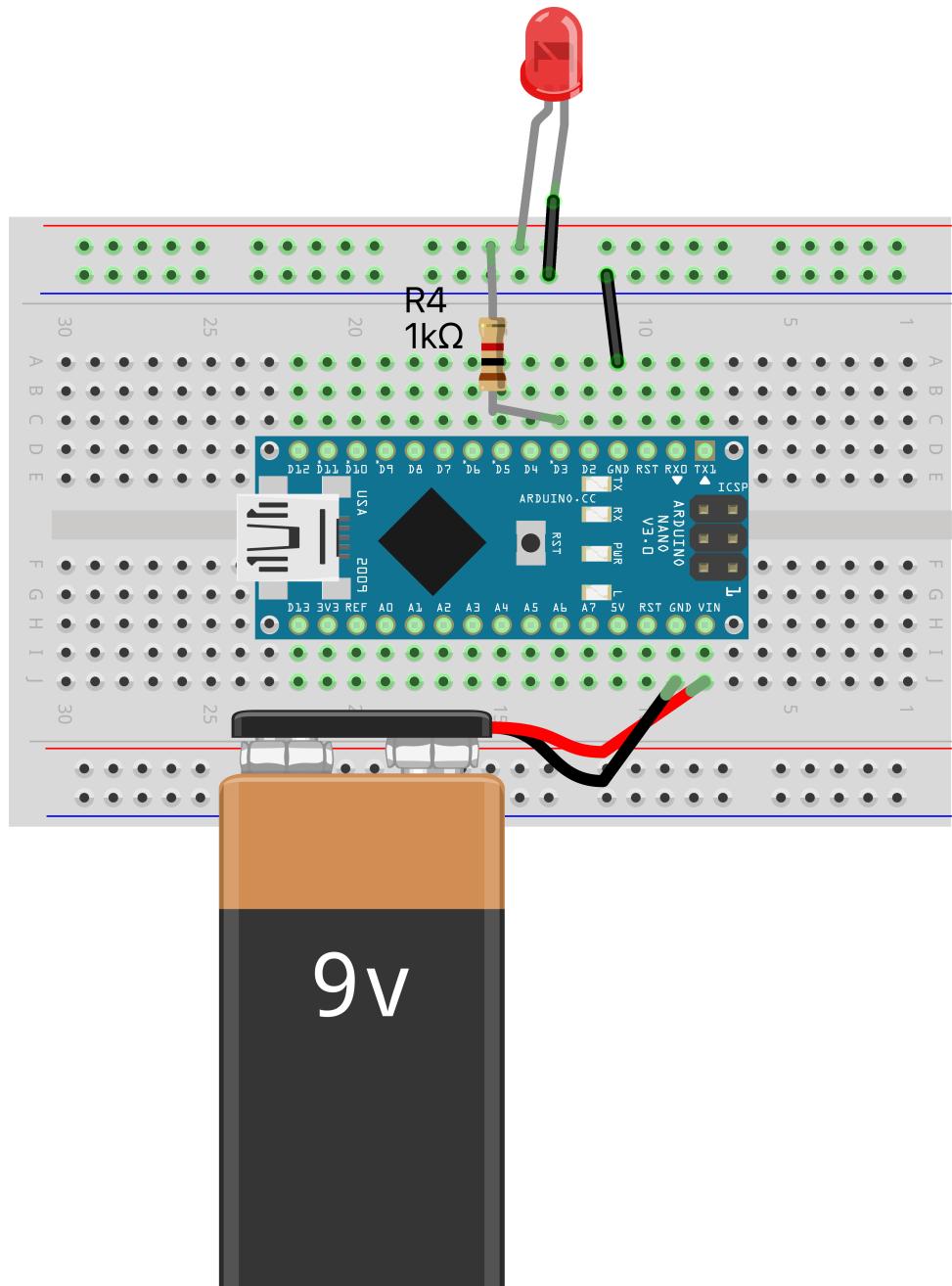



Blinking LED

Connect an LED to pin 3. Blinks the LED on and off.




Fading LED

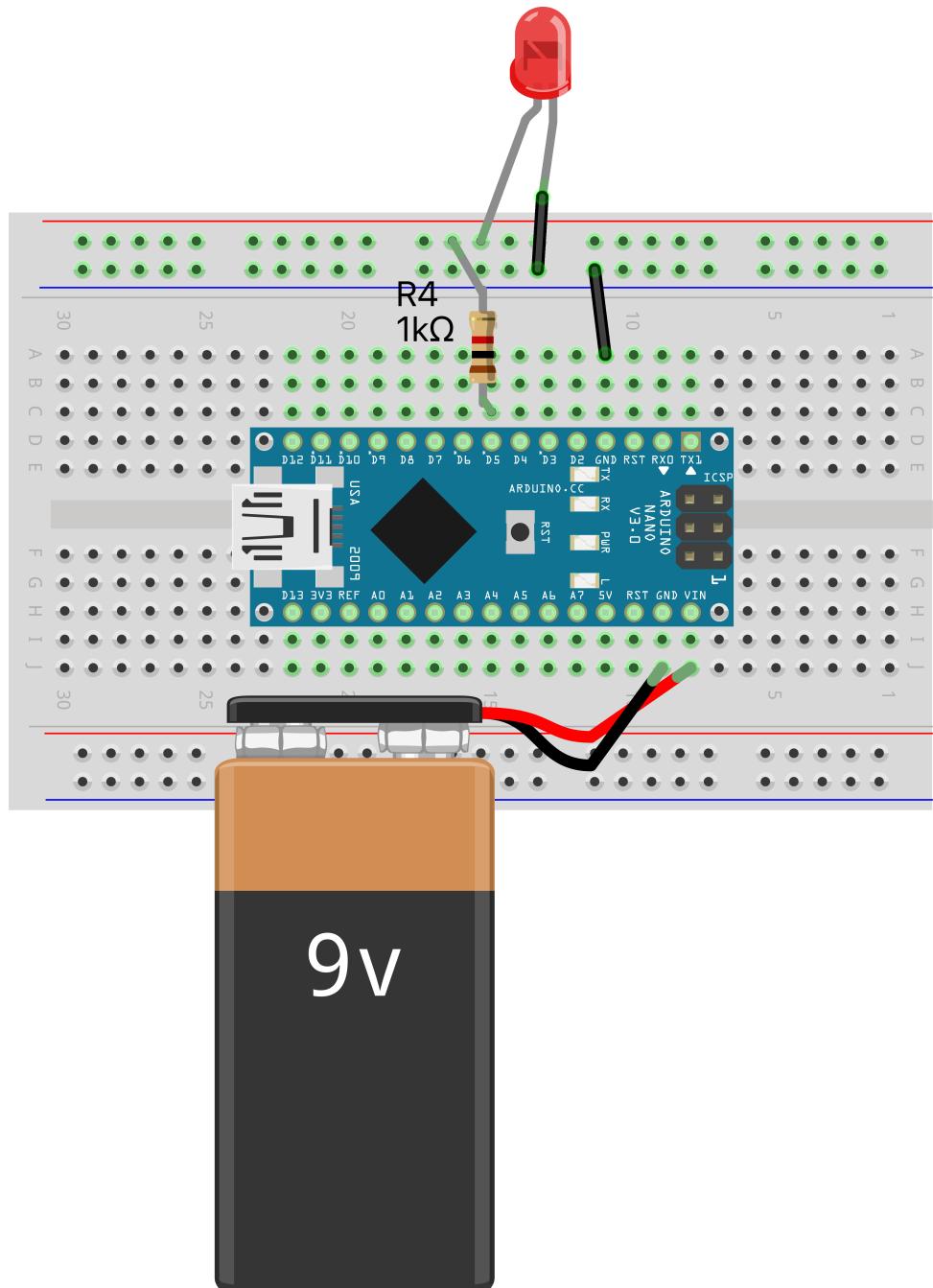Connect an LED to pin 5. Gradually change the LED brightness.



DC Motor

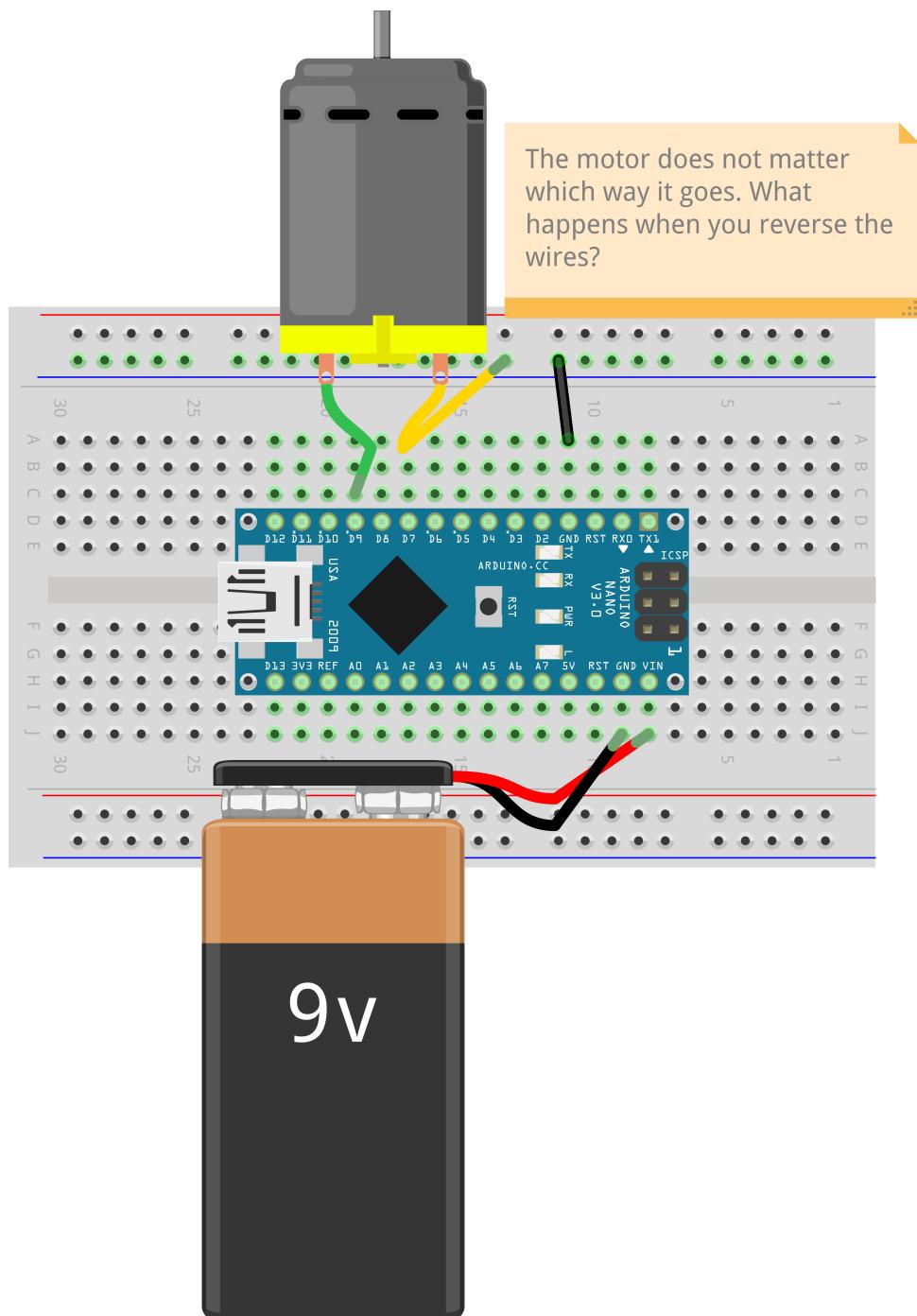
Connect a DC motor to pin 9. Controls the motor speed and direction.



fritzing

Slide Switch Control

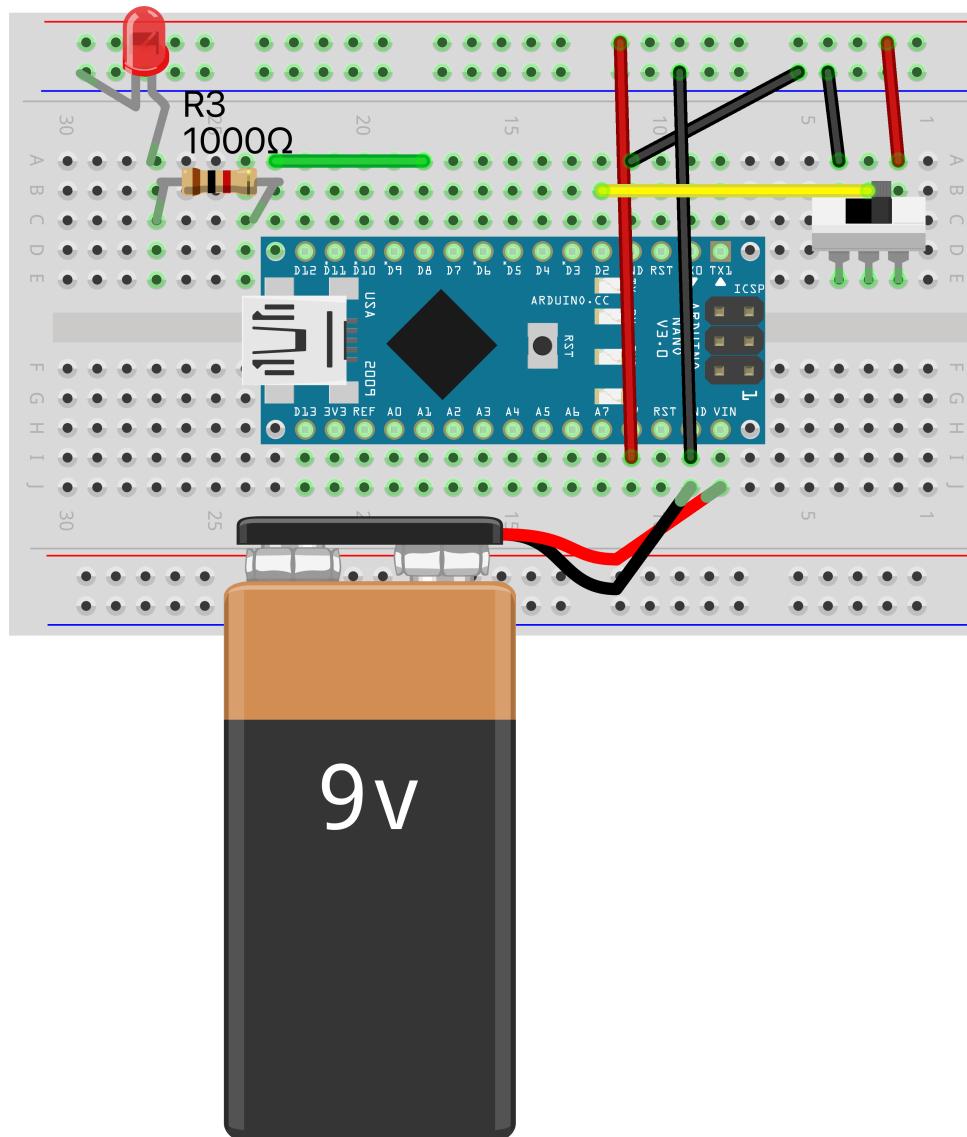
Connect a slide switch to pin 2. Connect an LED to pin 8. Toggle an LED with the switch.



fritzing

Push Button Control

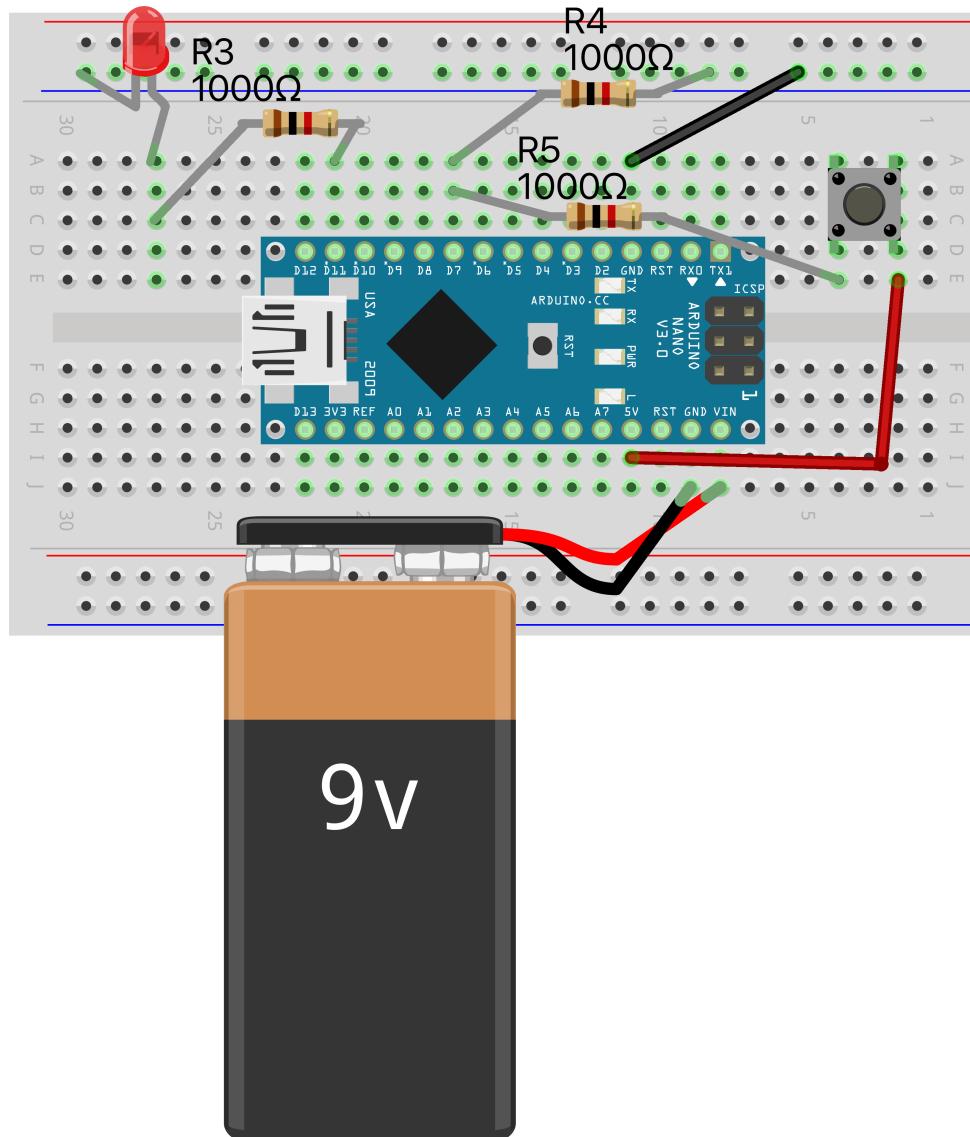
Connect a push button to pin 7. Connect an LED to pin 11. Controls an LED with the button.



fritzing

Photoresistor Control

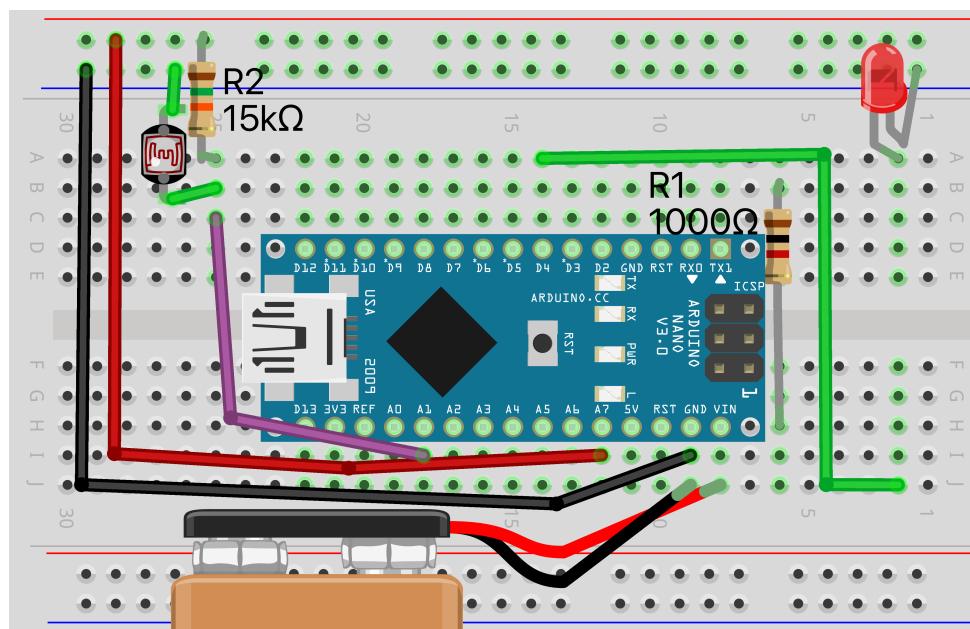
Connect a photoresistor to A1. Connect an LED to pin 4. Turns on an LED based on light levels near photoresistor.



fritzing

Potentiometer Control

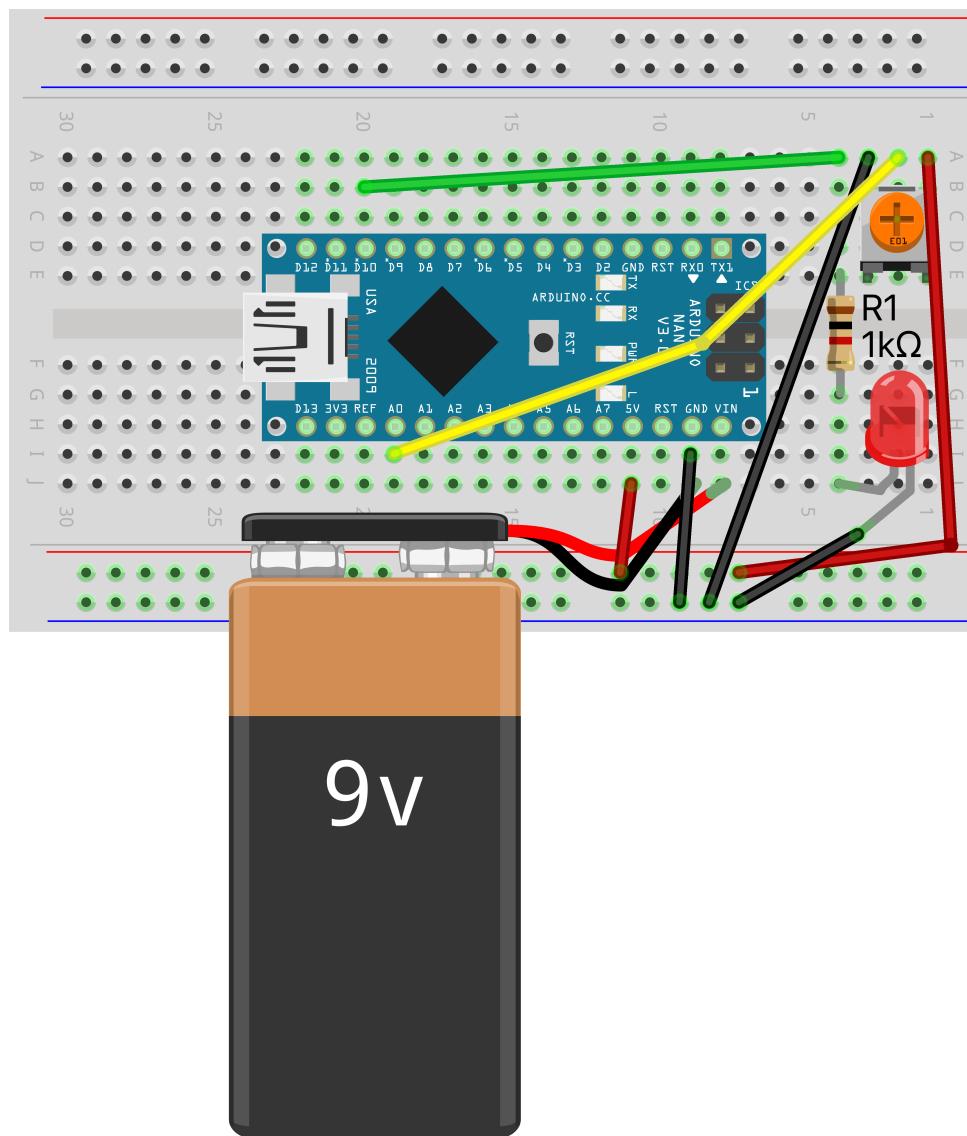Connect a potentiometer to A0. Connect an LED to pin 10. Adjusts LED brightness with the potentiometer.



fritzing